

# UWA – ENSC2003 Engineering Electrical Fundamental

Please complete your details below:

Surname: <u>Wilson</u>	Given Name: <u>Aden</u>
Student ID: <u>23100559</u>	Signature: <u>[Signature]</u>
<b>12:00PM, Thursday, September 15</b>	
<b>Class Test 2 (OPEN BOOK)</b>	
Time allowed: 40 minutes	This paper contains:
Max mark: 30	3 short questions and
Assessment Weight: 7%	4 calculation questions

Candidates should attempt all questions and show all working with numerical answers to 2 decimal places, show as much working as possible to gain maximum marks. You can use the blank pages for rough working, but these pages will not be marked.

Your test paper will be returned back to you in the week 9 practical class. Indicate below the day and time of your practical class. Select ONE only.

- |   |  |
|---|--|
| <input checked="" type="checkbox"/> Tuesday 3-5PM | <input type="checkbox"/> Friday 11AM-1PM |
| <input type="checkbox"/> Wednesday 8-10AM         | <input type="checkbox"/> Friday 2-4PM    |
| <input type="checkbox"/> Wednesday 11AM-1PM       | <input type="checkbox"/> Friday 4-6PM    |
| <input type="checkbox"/> Thursday 10AM-12PM       | <input type="checkbox"/> I don't know    |

Test Marker Use Only								
Short Questions			Calculation Questions				Total (/30)	Marker
Q1(/2)	Q2(/2)	Q3(/2)	Q1(/6)	Q2(/6)	Q3(/6)	Q4(/6)		
1	3		5	4	3.5	3	18.5	

## Part A: Short Questions

**Short Question 1.** A capacitor has a stored energy of  $500\mu J$  and a capacitance of  $0.15\mu F$ . Calculate the voltage (in volts) across this capacitor. (2 marks)


Write your answer(s) in the answer box below. Keep 2 decimal places in numeric answer. No unit is needed

Short Question 1  
Answer:

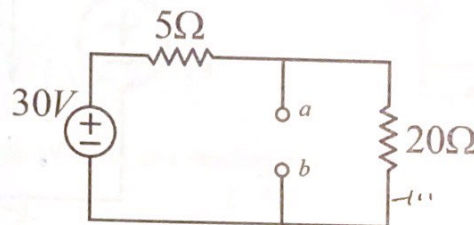81. 82 V

clear

**Short Question 2.** In the circuit shown below, calculate the Thevenin equivalent resistance  $R_{Th}$ , the Thevenin equivalent voltage  $V_{Th}$  and the Norton equivalent current  $I_N$  with respect to the open terminals a and b. (2 marks)




Write your answer(s) in the answer box below. Keep 2 decimal places in numeric answers.

Short Question 2  
Answer:

$R_{Th}$ :	4	Ω
$V_{Th}$ :	<del>6</del>	volts
$I_N$ :	<del>1.5</del>	amperes

~~1.5~~ + 1  
 $V = IR$   $I = \frac{V}{R}$

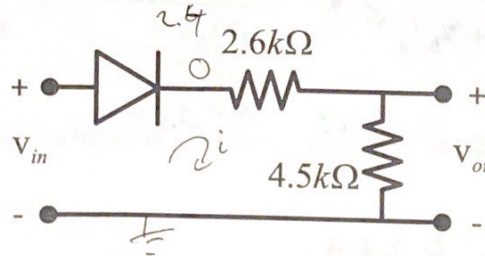**Short Question 3.** Consider the circuit below. Assuming the piecewise linear model for the diode and  $V_{D,on} = 0.6V$ , determine the value of  $v_{out}$  for each of the values of (a)  $v_{in} = +0.6V$ , and (b)  $v_{in} = +3.0V$ . (2 marks)



Handwritten calculation:  
 $-3 + 0.6 + 2.6i + 4.5i = 0$

Write your answer(s) in the answer box below. Keep 2 decimal places in numeric answers.

Short Question 3  
Answer:

(a) when $v_{in} = +0.6V$ ,	
$v_{out}$ :	0 volts
(b) when $v_{in} = +3.0V$ ,	
$v_{out}$ :	<del>1.5</del> volts


+ 1


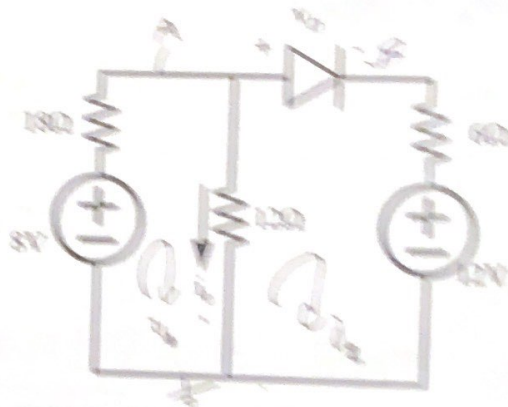
## Part B: Calculation Questions

Calculation Question 1. Assuming the piecewise linear model for the diode and  $V_{D,on} = 0.6V$ , determine the voltage across the diode  $v_D$  and the current through the  $12\Omega$  resistor  $i_D$  in the circuit given below. (6 marks)

Note: State all assumptions explicitly, show all your works clearly, sketch necessary circuit diagram(s) and label all details in sketch(es). Keep 2 decimal places in numeric answers.



Assume  $v_D$  is on

$$i_D = i_1 - i_2$$

$$KCL: 4.9 - 8 + 18i_1 + 6(i_1 - i_2) = 0$$

$$30i_1 = 12i_2 + 8$$

$$KVL: 12(i_1 - i_2) + 0.6 + 6i_2 + 12 = 0$$

$$18i_1 = 12i_2 - 11.4 \rightarrow 5i_1 + 0.45 = i_2$$

$$30(1.5i_2 + 0.45) = 12i_2 + 8$$

$$45i_2 + 28.5 = 12i_2 + 8$$

$$33i_2 = -20.5 \quad i_2 = -0.62 \quad \therefore \text{diode is off}$$

$$\text{At } i_1: \frac{5-8}{18} = \frac{4.9-8}{18} + i_D \quad i_D = 0 \rightarrow \text{diode is off}$$

$$\frac{5-8}{18} = \frac{4.9}{18} \quad \frac{8}{18} = \frac{4.9}{18} + \frac{4.9}{18} \quad A = 3.2V$$

$$i_D = \frac{4.9-0}{18} = \frac{3.2}{18} = 0.27A$$

$$\text{At } i_2: \frac{12-8}{6} = 0 \quad \therefore i_2 = 0$$

$$v_D = 4.9 - 3.2V$$


Calculation Question 2. Given the operational amplifier circuit shown below, answer the following questions. Assume that the operational amplifier is ideal. (6 marks)

Note: State assumptions and rules clearly and explicitly. Show all your works, sketch necessary circuit diagram(s) and label all details in sketch(-es). Keep 2 decimal places in numeric answers.

Assumptions

$$V_+ = V_-$$

$$I_+ = I_- = 0$$

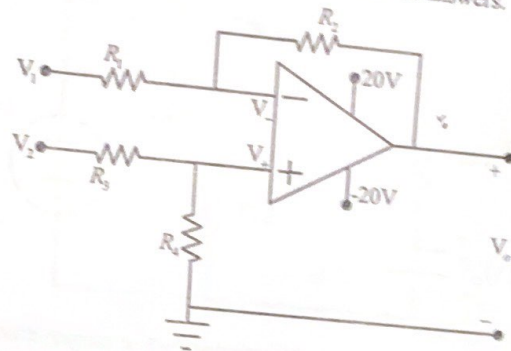

- (a) Determine an expression for  $V_-$  as a function of  $V_1$ ,  $V_2$ ,  $V_o$  and the circuit resistance. (2 marks)

$$\frac{V_1 - V_-}{R_1} = \frac{V_- - V_o}{R_2} + I_- \quad \text{as } I_- = 0$$

$$\frac{V_1}{R_1} + \frac{V_o}{R_2} = \frac{V_-}{R_2} + \frac{V_-}{R_1}$$

$$V_- = \frac{\frac{V_1}{R_1} + \frac{V_o}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{\frac{R_2 V_1 + R_1 V_o}{R_1 R_2}}{\frac{R_1 + R_2}{R_1 R_2}} = \frac{R_2 V_1 + R_1 V_o}{R_1 + R_2}$$

- (b) Determine an expression for  $V_+$  as a function of  $V_1$ ,  $V_2$ ,  $V_o$  and the circuit resistance. (2 marks)

$$\frac{V_2 - V_+}{R_3} = \frac{V_+ - 0}{R_4}$$

$$\frac{V_2}{R_3} = \frac{V_+}{R_4} + \frac{V_+}{R_3} \quad V_+ = \frac{V_2}{\frac{1}{R_3} + \frac{1}{R_4}} = \frac{V_2}{\frac{R_3 + R_4}{R_3 R_4}} = \frac{V_2 R_3 R_4}{R_3 + R_4}$$


(c) Determine  $V_o$  given that  $\frac{R_2}{R_1} = \frac{R_4}{R_3} = 1000$ ,  $V_1 = 0.1V$  and  $V_2 = 0.15V$ . (2 marks)






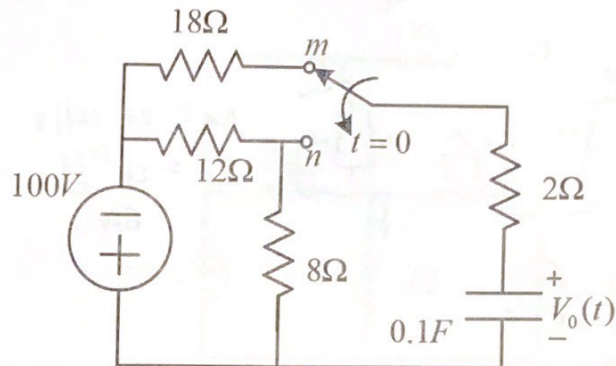3.5/6

**Calculation Question 3.** In the circuit shown below, the switch has been in the position *m* for a very long time. The switch moves to the position *n* at  $t=0$  and remains there indefinitely. (6 marks)  
**Note:** Show all your works, sketch necessary circuit diagram(s) and label all details in sketch(-es). Keep 2 decimal places in numeric answers.





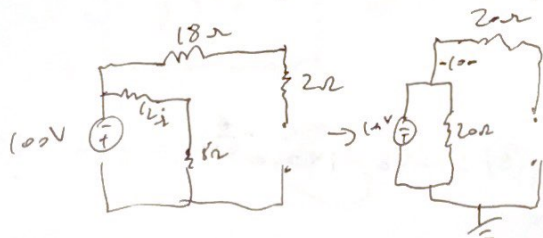(a) Determine the Thevenin equivalent circuit with respect to the capacitor when  $t < 0$ . (2 marks)




$$R_{eq} = 20 + 20 = 40\Omega$$
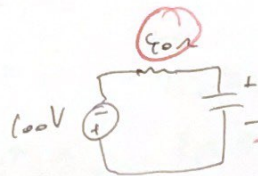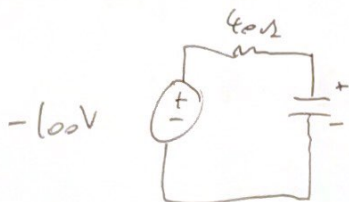
$$V_{Th} = \frac{100 \times 20}{20 + 20} = 50V$$




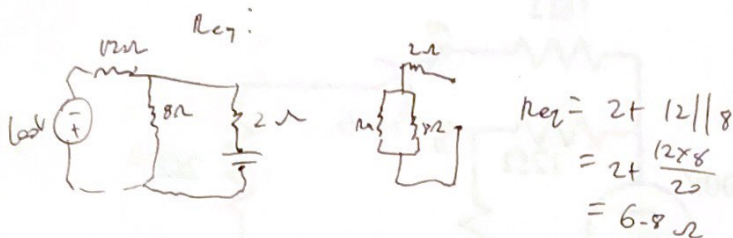(b) Determine the mathematical expression of the voltage across the capacitor, i.e.  $V_0(t)$ , for  $t \geq 0$ . (4 marks)

$\tau: t > 0 \quad C_{eq} = 0.1 \text{ F} \quad \tau = RC = 0.068$




$V_0: t < 0$

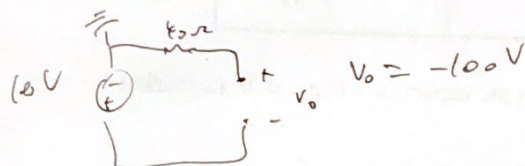

$V_0: t > 0$

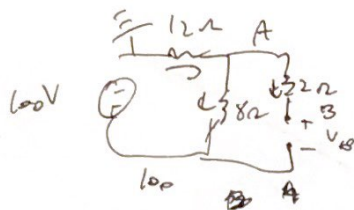$V_0(t) = -40 - 140 e^{-\frac{t}{0.068}}$



+2.5

@ A  $\frac{0-A}{12} = \frac{A-100}{8} + \frac{A-B}{2}$

@ B  $\frac{A-B}{2} = 0$

$A=B$

$-\frac{A}{12} = \frac{A-100}{8} + 0$

$\frac{100}{8} = \frac{A}{8} + \frac{A}{12}$



$A = 60 \text{ V}$

$V_0 = 60 - 100$

$= -40 \text{ V}$

3/6  
**Calculation Question 4.** For the circuit shown below, use the superposition theorem to find current  $i$ . (6 marks)

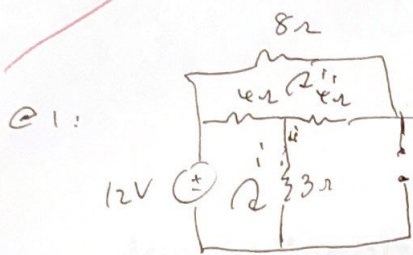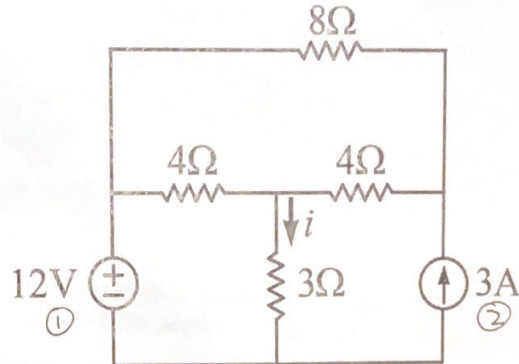**Note:** Show all your works, sketch necessary circuit diagram(s) and label all details in sketch(-es). Keep 2 decimal places in numeric answers.



$$\text{Q1: } -12 + 4(i - i_1) + 3i = 0 \quad 7i = 12 + i_1$$

$$\text{Q1: } 4i_1 + 4(i_1 - i) + 8i_1 = 0$$

$$8i_1 - i = 0 \quad 16i_1 = i$$

$$i = 1.73 \text{ A}$$

$$7i = 12 + i_1$$

$$7i = 12 + i_1$$

$$14i = 12 + 2i_1$$

$$12i = 12 + i_1$$

$$i_1 = 0.08$$

Q2



$$i_3 = -3 \text{ A}$$